



Title of Discipline:

# Computer-Aided Analysis of Electronic Circuits

## Laboratory Lecture 3

Bachelor : Telecommunication Technologies and Systems

Year of Study: 2

# Computer-Aided Analysis of Electronic Circuits

## Laboratory 3

The description of the passive analog devices  
supported by PSpice A/D

## Analog Device Types

*There are different types of analog devices supported by Pspice A/D.*

- analog primitives,*
- independent and controlled sources,*
- subcircuit calls.*

*The device declaration begins with the name of the individual device.*

*The **first letter** of the name determines the **device type**. What follows the name depends on the device type and its requested characteristics.*

# Analog Device Summary

Passive device	Independent sources	Controlled sources	Controlled switch	Semiconductors
R – Resistor C – Capacitor L – Inductor K – Inductor coupling T – Transmission line	V – Independent voltage source I – Independent current source	E – Voltage-controlled voltage source G – Voltage-controlled current source F – Current-controlled current source H – Current-controlled voltage source	S – Voltage-controlled switch W – Current-controlled switch	D – Diode Q – Bipolar transistor J – Junction FET M – MOSFET B – GaAsFET

# Passive Devices

## ***Resistor***

### General form

R<name> <N+> <N-> [model name] <value> [TC = <TC1> [, <TC2>]]

### Examples

Rs 12 0 1.5k

R3 2 9 7.5k TC=0.015,-0.003

Rfdbck 5 17 RMOD 5k

### Model form

.MODEL <model name> RES [model parameters]

# Passive Devices

## Resistor model parameters

Model parameter	Description	Units	Default
R	resistance multiplier	-	1.0
TC1	linear temperature coefficient	$^{\circ}\text{C}^{-1}$	0.0
TC2	quadratic temperature coefficient	$^{\circ}\text{C}^{-2}$	0.0
TCE	exponential temperature coefficient	$\%/^{\circ}\text{C}$	0.0

# Passive Devices

## Arguments and options

<N+> <N-> are the nodes. Positive current flows from <N+> node through the resistor to the <N-> node.

## Resistor value formulas

If [model name] is included and TCE is specified, then the resistance is given by:

$$R_{\text{total}} = \langle \text{value} \rangle \cdot R \cdot 1.01^{\text{TCE} \cdot (T - T_{\text{nom}})}$$

If [model name] is included and TCE is not specified, then the resistance is given by:

$$R_{\text{total}} = \langle \text{value} \rangle \cdot R \cdot (1 + \text{TC1} \cdot (T - T_{\text{nom}}) + \text{TC2} \cdot (T - T_{\text{nom}})^2)$$

Where <value> is the one from the general form of the resistor. Tnom is the nominal temperature.

## Resistor equation for noise

Noise is calculated assuming a 1.0-hertz bandwidth. The resistor generates thermal noise using the following spectral power density ( per unit bandwidth):

$$i^2 = 4 \cdot k \cdot T / R_{\text{total}}$$

# Passive Devices

## ***Capacitor***

### General form

C<name> <N+> <N-> [model name] <value> [IC = <initial value>]

### Examples

Cref 12 0 220u

C5 3 8 47nF IC=2.5V

Cfdbck 2 24 CMOD 100pF

### Model form

.MODEL <model name> CAP [model parameters]



# Passive Devices

## Capacitor model parameters

Model parameter	Description	Units	Default
C	capacitance multiplier	-	1.0
TC1	linear temperature coefficient	$^{\circ}\text{C}^{-1}$	0.0
TC2	quadratic temperature coefficient	$^{\circ}\text{C}^{-2}$	0.0
VC1	linear voltage coefficient	volt <sup>-1</sup>	0.0
VC2	quadratic voltage coefficient	volt <sup>-2</sup>	0.0

# Passive Devices

## Arguments and options

<N+> <N-> are the nodes. The voltage across the component is defined as the first node voltage, less the second node voltage. If [model name] is left out, then <value> is the capacitance in farads.

The initial voltage across the capacitor during the bias point calculation. It can also be specified in a circuit file using a .IC command as follows:

```
.IC V( N+, N- ) <initial value>
```

## Capacitor value formula

If [model name] is specified, then the value is given by:

$$C_{\text{total}} = \langle \text{value} \rangle \cdot C \cdot (1 + \mathbf{VC1} \cdot V + \mathbf{VC2} \cdot V^2) \cdot (1 + \mathbf{TC1} \cdot (T - T_{\text{nom}}) + \mathbf{TC2} \cdot (T - T_{\text{nom}})^2)$$

Where <value> is the one from the general form of the capacitor. Tnom is the nominal temperature.

# Passive Devices

## *Inductor*

General form:

L<name> <N+> <N-> [model name] <value> [IC = <initial value>]

Examples

Lload 16 0 22mH

L2 2 11 100uH IC=3mA

Lsec 13 17 LMOD 10uH

Model form

.MODEL <model name> IND [model parameters]

# Passive Devices

## Inductor model parameters

Model parameter	Description	Units	Default
L	inductance multiplier	-	1.0
TC1	linear temperature coefficient	$^{\circ}\text{C}^{-1}$	0.0
TC2	quadratic temperature coefficient	$^{\circ}\text{C}^{-2}$	0.0
IL1	linear current coefficient	$\text{amp}^{-1}$	0.0
IL2	quadratic current coefficient	$\text{amp}^{-2}$	0.0

# Passive Devices

## Arguments and options

<N+> <N-> are the nodes. The voltage across the component is defined as the first node voltage, less the second node voltage. If [model name] is left out, then <value> is the capacitance in farads.

<initial value> is the initial current through the inductor during the bias point calculation. It can also be specified in a circuit file using a .IC command as follows:

```
.IC I( L<name>) <initial value>
```

## Inductor value formula

If [model name] is specified, then the effective value is given by:

$$L_{\text{total}} = \langle \text{value} \rangle \cdot L \cdot (1 + \mathbf{IL1} \cdot I + \mathbf{IL2} \cdot I^2) \cdot (1 + \mathbf{TC1} \cdot (T - T_{\text{nom}}) + \mathbf{TC2} \cdot (T - T_{\text{nom}})^2)$$

Where <value> is the one from the general form of the inductor. Tnom is the nominal temperature.

# Passive Devices

## *Inductor coupling*

### General form

K<name> L<inductor name> <L<inductor name>> \* <coupling value>

K<name> <L<inductor name>>\* <coupling value> <model name>

### Examples

K12 L1 L2 0.95

Ktransf Lpr Lsec 1

Kcore L1 L2 L3 L4 0.98 MODCORE

### Model form

.MODEL <model name> CORE [model parameters]

# Passive Devices

## Arguments and options

K<name> L <inductor name>

Couples two or more inductors.

<coupling value> This is the coefficient of mutual coupling, which must be between -1.0 and 1.0.

This coefficient is defined by the equation

$$\text{< coupling value >} = M_{ij}/(L_i \cdot L_j)^{1/2}$$

Where

$L_i, L_j$  = a coupled-[air of inductors

$M_{ij}$  = the mutual inductance between  $L_i$  and  $L_j$

# Passive Devices

## Transmission line

### Description

The transmission line device is a bidirectional delay line with two ports, A and B.

### Ideal transmission line

#### General form

T<name> < NA+> <NA-><NB+><NB-> [model name]  
 + Z0 = <value> [TD = <value>] [ F = <value> [NL =<value>]]

where

NA+, NA-, NB+, NB- are nodes of port A, respectively B.

Z0 is the characteristic impedance.

The transmission line's length can be specified either by TD, a delay in seconds, or by F and NL, a frequency and a relative wavelength at F.

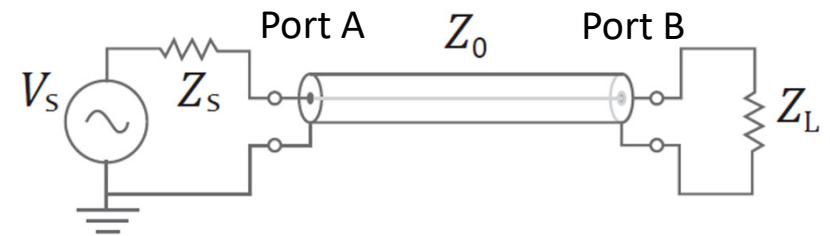


Figure 1: A typical transmission line circuit



# Passive Devices

## *Lossy transmission line*

General form

T<name> <NA+> <NA-><NB+><NB-> [ <model name> [electrical length value]]


+ LEN = <value> R = <value> L = <value> G = <value> C = <value>

where

NA+, NA-, NB+, NB- are nodes of port A, and B respectively.

LEN is the electrical length.

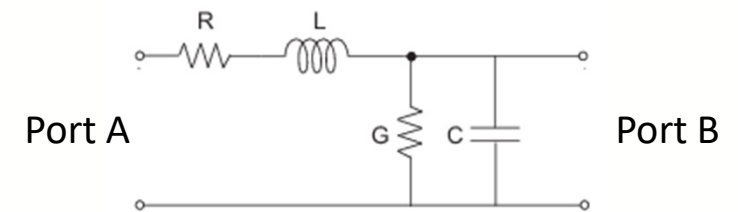R, L, G, and C are the per unit length values of resistance, inductance, conductance, and capacitance, respectively.




Model form

.MODEL <model name> TRN [model parameters]

# Applications
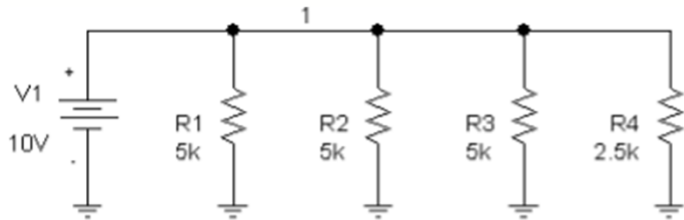
## Application 1 – description and analysis of a circuit with different resistor models



### Resistor model parameters:

R1: no variation with temperature

R2: TC1=0.01;

R3: TC1=0.01, TC2=-0.5e-3;


R4: R=2, TCE=2.

### Activities:

- Describe the circuit into the SPICE circuit file (.cir). For each of resistors R2, R3 and R4 specify a model name and define them with .MODEL command.
- Add voltage source as follow: V1 1 0 10
- Add .DC command to perform a DC analysis when the temperature is swept in the interval -25°C...75°C with step size of 2°C.  
.DC TEMP -25 75 2
- Perform the simulation
- In the **Probe** graphic analyzer plot the resistances of those four resistors by entering the following expressions:  
 $V(1)/I(R1)$ ,  $V(1)/I(R2)$ ,  $V(1)/I(R3)$ ,  $V(1)/I(R4)$
- What is the temperature value at which all resistors have the same value?

# Applications
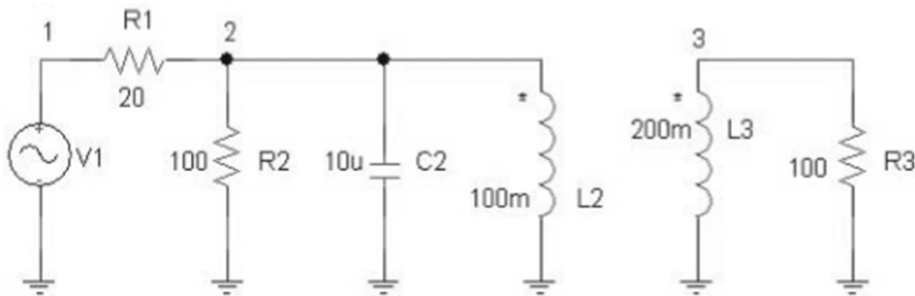
## Application 2 – description and analysis of a RLC circuit



### Circuit details:

C2: initial condition = 0.5V

L2: initial condition = 0.3A

Coupling coefficient between L2 and L3 is 1

V1: V1 1 0 SIN(0 1 500)

### Activities:

- Describe the circuit into the SPICE circuit file .cir
- Add the .TRAN command to perform a transient analysis  
.TRAN 0.1m 6m 0 50u
- Perform the simulation
- Show and inspect the waveforms of the voltages V(1), V(2) and V(3) in the **Probe** graphic analyzer. Determine the amplitude of V(2) and V(3).
- Show and inspect in a separate plot the waveforms of the currents through L2 and L3.